

3. Referat 1 CEL

Dioda semiconductoare si redresoare monofazate

Nume	Grupa	Data

$R_{d1} =$

$R_{d2} =$

Tabel 1

Dioda redresoare, caracteristica directă

I_D	mA	0	0,5	1	2	5	10	20	50	100	200
U_D	V	0									
R_d	Ω										

$I_{S1} =$

$I_{S2} =$

$R_{prim} =$

$R_{sec1} =$

$R_{sec2} =$

Tabel 2

Caracteristica redresor monoalternanta fara filtru

R (k Ω)	∞	12	2,7	0,560	0,150	0,047
I (mA)						
U (V)						

Monoalternanță:

$U_M =$

T =

f =

Dublă alternanță:

$U_M =$

T =

f =

Tabel 3

Caracteristica redresor monoalternanta cu filtru

R (k Ω)	∞	12	2,7	0,560	0,150	0,047
I (mA)						
U (V)						
U_M (V)						
U_m (V)						

Monoalternanță: $U_M =$

T =

f =

ΔU masurat=

ΔU calculat=

Calcul ΔU :

Dublă alternanță: $U_M =$

T =

f =

ΔU masurat=

ΔU calculat=

Calcul ΔU :

Observații: