

Hazard

	X_1	X_2	X_3	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

1. Se calculeaza functia ce trebuie implementata:

a. SI-NU

Se calculeaza FMD si se aplica De Morgan (se neaga de doua ori).

b. SAU-NU

Se calculeaza FMC si se aplica De Morgan (se neaga de doua ori).


$t_{p2} < t_{p3}$
 $X_1=1, X_2=0$

$$\overline{f}^{FMD} = \sum (1, 4, 5, 6) = \overline{X_1} \overline{X_2} X_3 + X_1 \overline{X_2} X_3 + X_1 X_2 \overline{X_3}$$

$$\overline{f}^{FMD} = X_2 \overline{X_3} + \overline{X_2} X_3$$


$$\overline{f}^{FMC} = \overline{\overline{X_1 + X_3} + \overline{X_2 + \overline{X_3}}}$$

2. Se scrie schema.

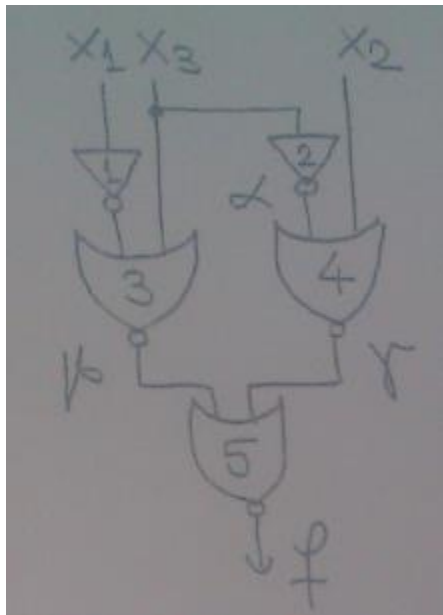

3. Se noteaza semnalele care ies din porti.

4. Se intocmesc graficele de timp.

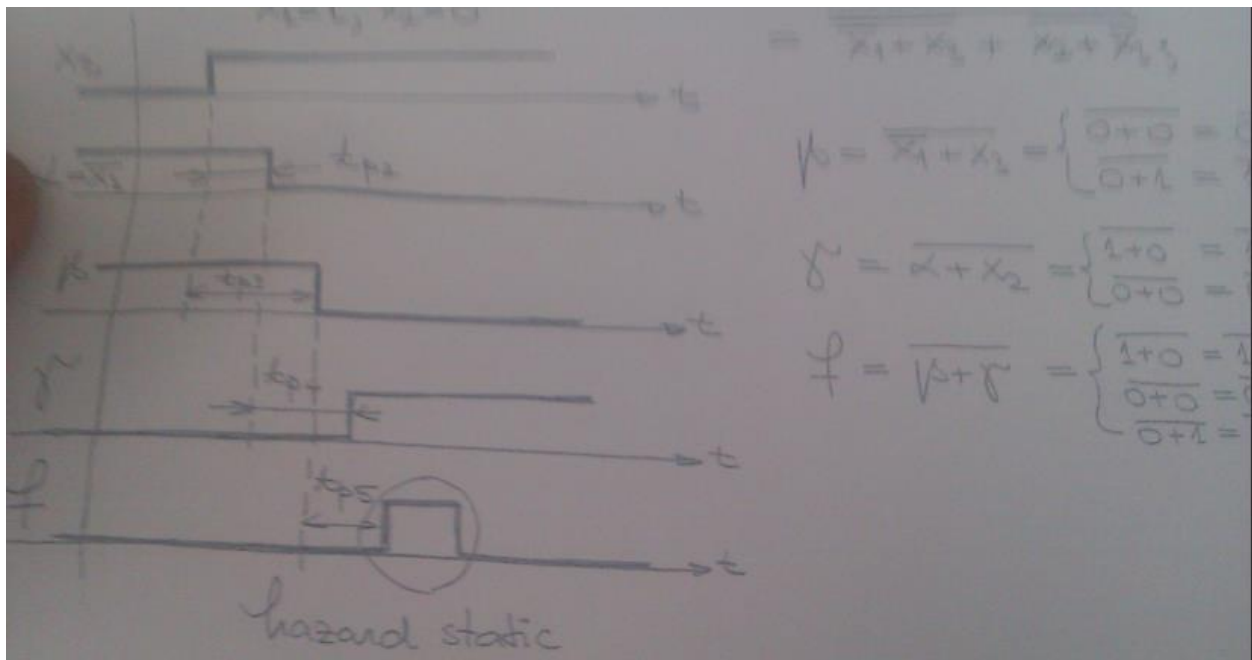

5. Se alege un termen redundant pentru eliminarea hazardului si se reface schema, cu linii intrerupte pentru poarta termenului redundant.

